

11 Worksheet


Intermediate level

- 1 A $30\ \mu\text{F}$ capacitor is connected to a $9.0\ \text{V}$ battery.
 - a Calculate the charge on the capacitor. [2]
 - b How many excess electrons are there on the negative plate of the capacitor? (Elementary charge $e = 1.6 \times 10^{-19}\ \text{C}$) [2]


- 2 The p.d. across a capacitor is $3.0\ \text{V}$ and the charge on the capacitor is $150\ \text{nC}$. Determine the charge on the capacitor when the p.d. is:
 - a $6.0\ \text{V}$ [2]
 - b $9.0\ \text{V}$. [2]

- 3 A $1000\ \mu\text{F}$ capacitor is charged to a potential difference of $9.0\ \text{V}$.
 - a Calculate the energy stored by the capacitor. [2]
 - b Determine the energy stored by the capacitor when the p.d. across it is doubled. [2]

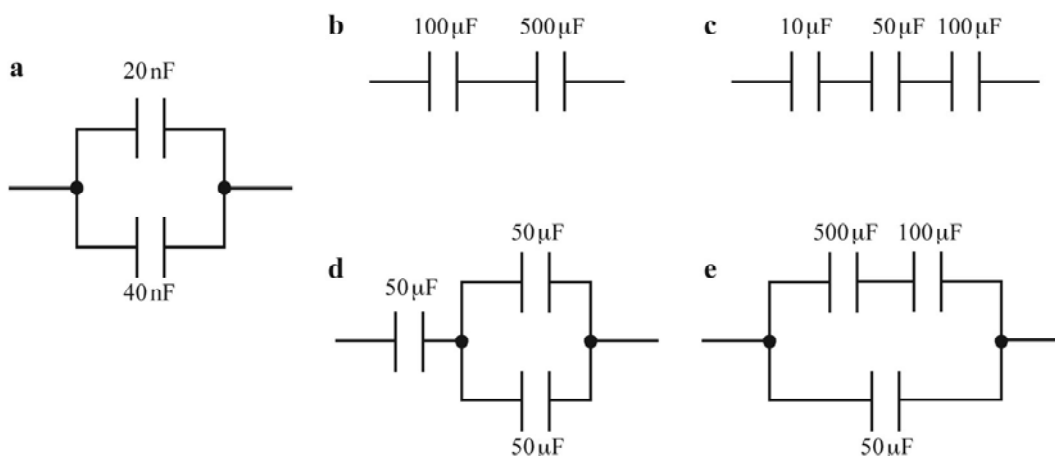- 4 For each circuit below, determine the total capacitance of the circuit. [14]



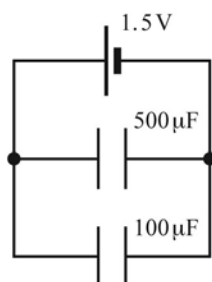
- 5 The diagram shows an electrical circuit.




- a Calculate the total capacitance of the two capacitors in parallel. [2]
- b What is the potential difference across each capacitor? [1]
- c Calculate the total charge stored by the circuit. [2]
- d Calculate the total energy stored by the capacitors. [2]

Higher level

- 6 A $10\,000\ \mu\text{F}$ capacitor is charged to its maximum operating voltage of $32\ \text{V}$. The charged capacitor is discharged through a filament lamp. The flash of light from the lamp lasts for $300\ \text{ms}$.
- Calculate the energy stored by the capacitor. [2]
 - Determine the average power dissipated in the filament lamp. [2]
- 7 The diagram shows a $1000\ \mu\text{F}$ capacitor charged to a p.d. of $12\ \text{V}$.
- Calculate the charge on the $1000\ \mu\text{F}$ capacitor. [2]

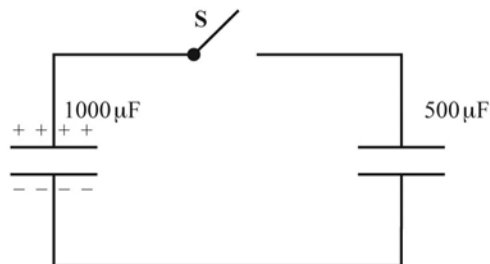

- The $1000\ \mu\text{F}$ capacitor is connected across an uncharged $500\ \mu\text{F}$ capacitor by closing the switch **S**. The charge initially stored by the $1000\ \mu\text{F}$ capacitor is now shared with the $500\ \mu\text{F}$ capacitor.
 - Calculate the total capacitance of the capacitors in parallel. [2]
 - Show that the p.d. across each capacitor is $8.0\ \text{V}$. [2]
- 8 A charged capacitor is connected across a resistor of resistance $100\ \text{k}\Omega$. The graph below shows the variation of p.d. V across the capacitor with time t .

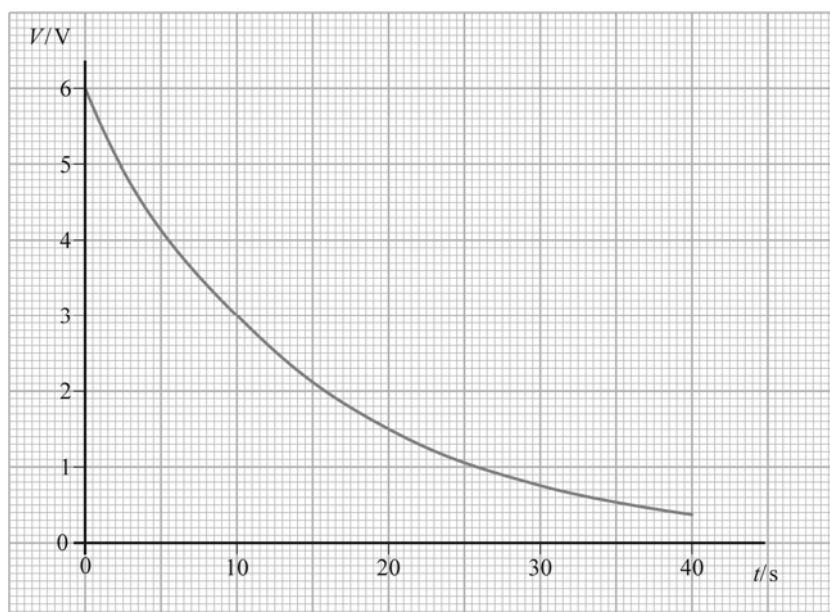


Use the graph to determine:

- the initial current in the circuit [2]
- the time constant of the circuit [2]
- the capacitance C of the capacitor. (Hint: use your answer to **b**.) [2]

- 9 A $220\ \mu\text{F}$ capacitor is charged to a potential difference of $8.0\ \text{V}$ and then discharged through a resistor of resistance $1.2\ \text{M}\Omega$.
- Determine the time constant τ of the circuit. [2]
 - Calculate:
 - the initial current in the circuit [2]
 - the current in the circuit after a time equal to 2τ [2]
 - the p.d. across the capacitor after a time of $50\ \text{s}$. [3]

Extension

- 10 A $100\ \mu\text{F}$ capacitor is discharged through a resistor of resistance $470\ \text{k}\Omega$. Determine the 'half-life' of this circuit. (The half-life of the circuit is the time taken for the voltage across the capacitor to decrease to 50% of its initial value.) [5]
- 11 The diagram below shows a charged capacitor of capacitance C . When the switch **S** is closed, this capacitor is connected across the uncharged capacitor of capacitance $2C$. Calculate the percentage of energy lost as heat in the resistor and explain why the actual resistance of the resistor is irrelevant. [7]

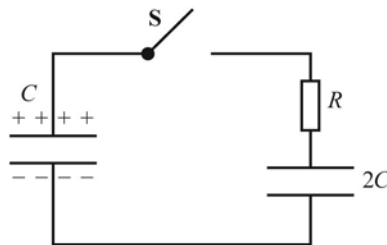

Total: Score: %
70